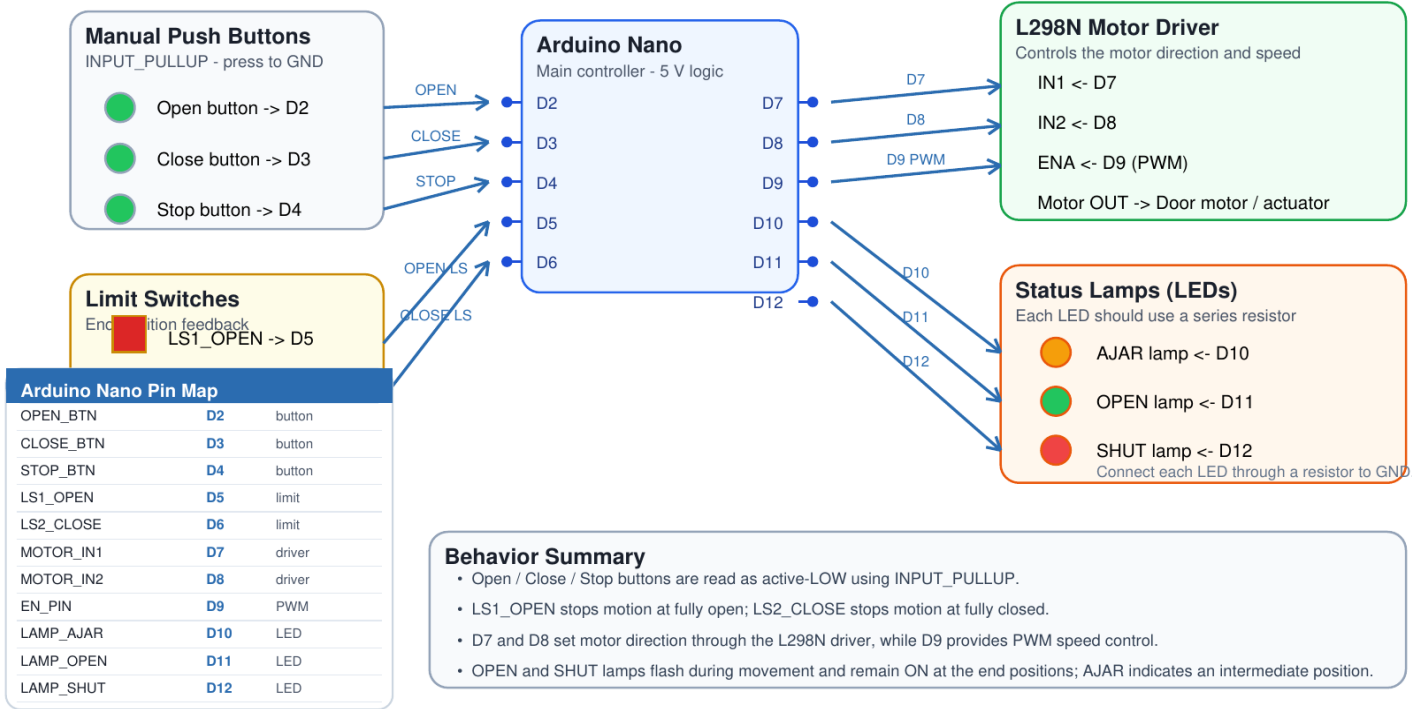


Arduino Nano Garage Door Diagram

Smart Garage Door Wiring Diagram - Arduino Nano

Diagram derived from the uploaded Arduino Nano code and user-provided project photos.



Prepared for GitHub portfolio documentation. Diagram is conceptual and follows the uploaded code logic.

Embedded diagram preview

Editable Wiring Table

Signal	Board Pin	Connects To	Purpose
OPEN_BTN	D2	Open push button	Manual open command
CLOSE_BTN	D3	Close push button	Manual close command
STOP_BTN	D4	Stop push button	Immediate stop command
LS1_OPEN	D5	Open limit switch	Detect fully open position
LS2_CLOSE	D6	Close limit switch	Detect fully closed position
MOTOR_IN1	D7	L298N IN1	Motor direction control
MOTOR_IN2	D8	L298N IN2	Motor direction control
EN_PIN	D9	L298N ENA (PWM)	Motor speed control
LAMP_AJAR	D10	Ajar indicator LED	Door partially open indication
LAMP_OPEN	D11	Open indicator LED	Fully open / opening indication
LAMP_SHUT	D12	Shut indicator LED	Fully closed / closing indication

Editable Notes

Topic	Value / Note
Motor driver	L298N with IN1, IN2, and ENA used by the Nano code.
Logic style	PLC-inspired prototype with Open / Close / Stop logic and status lamps.