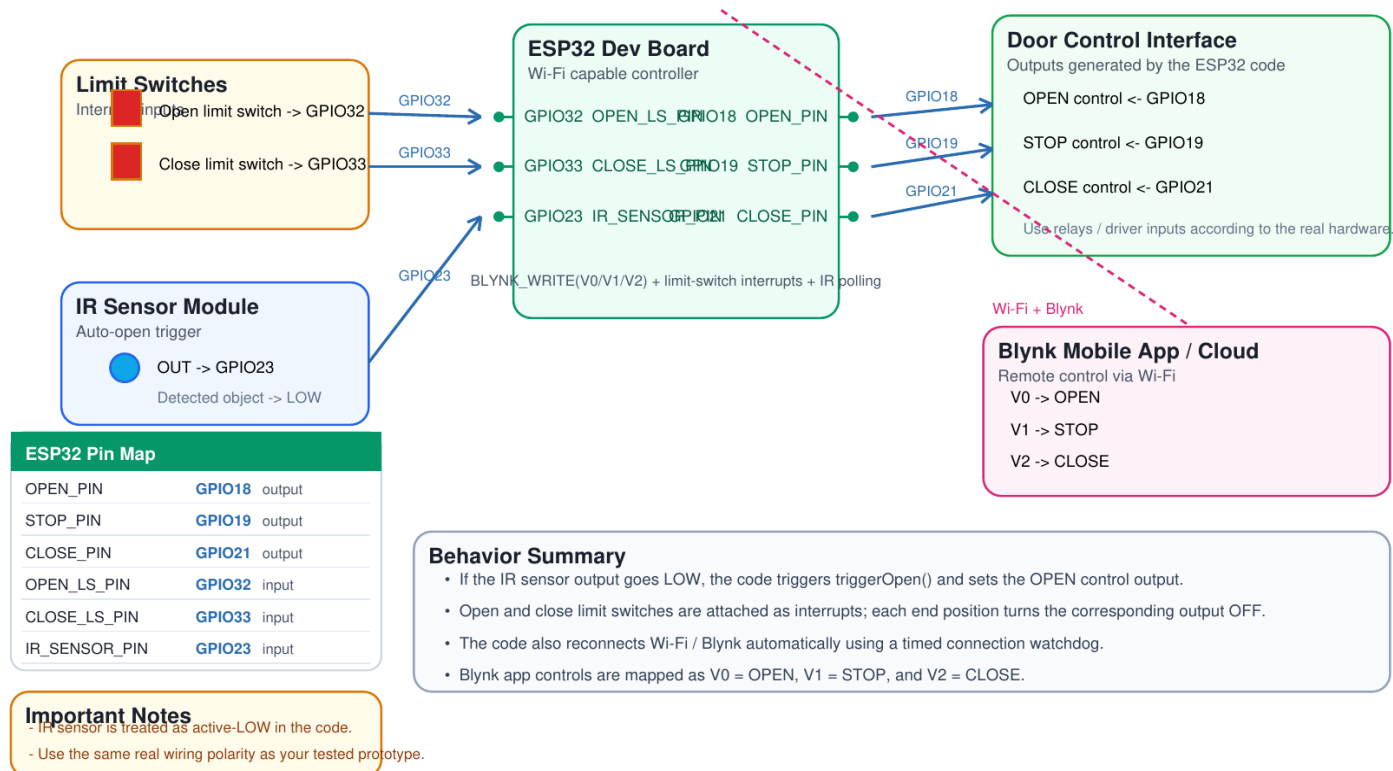


ESP32 + IR Garage Door Diagram

Smart Garage Door Wiring Diagram - ESP32 + IR

Diagram derived from the uploaded ESP32 code. Remote Blynk control and IR-based auto-open are included.



Prepared for GitHub portfolio documentation. Diagram is conceptual and follows the uploaded ESP32 code logic.

Embedded diagram preview

Editable Wiring Table

Signal	Board Pin	Connects To	Purpose
OPEN_PIN	GPIO18	Open relay / motor open control	Door opening command
STOP_PIN	GPIO19	Stop relay / motor stop control	Door stop command
CLOSE_PIN	GPIO21	Close relay / motor close control	Door closing command
OPEN_LS_PIN	GPIO32	Open limit switch	Detect fully open position
CLOSE_LS_PIN	GPIO33	Close limit switch	Detect fully closed position
IR_SENSOR_PIN	GPIO23	IR sensor OUT	Auto-open trigger when object is detected

Editable Notes

Topic	Value / Note
Controller	ESP32 board with Blynk-based remote control logic.
Sensor	IR sensor module used for automatic opening trigger.
Security	Keep Blynk token and Wi-Fi credentials outside the public repository.